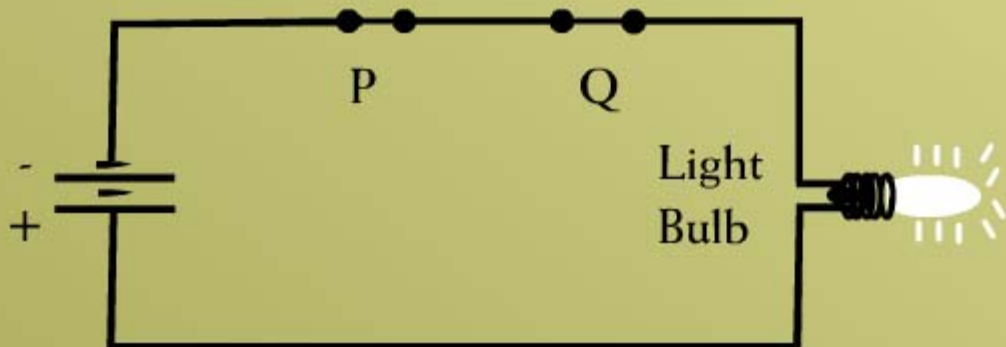



SWITCHES IN SERIES



 open


 close

 open

SWITCHES IN SERIES

Switches		Light Bulb
P	Q	State
Open	Open	Off
Open	Closed	Off
Closed	Open	Off
Closed	Closed	On

SWITCHES IN PARALLEL

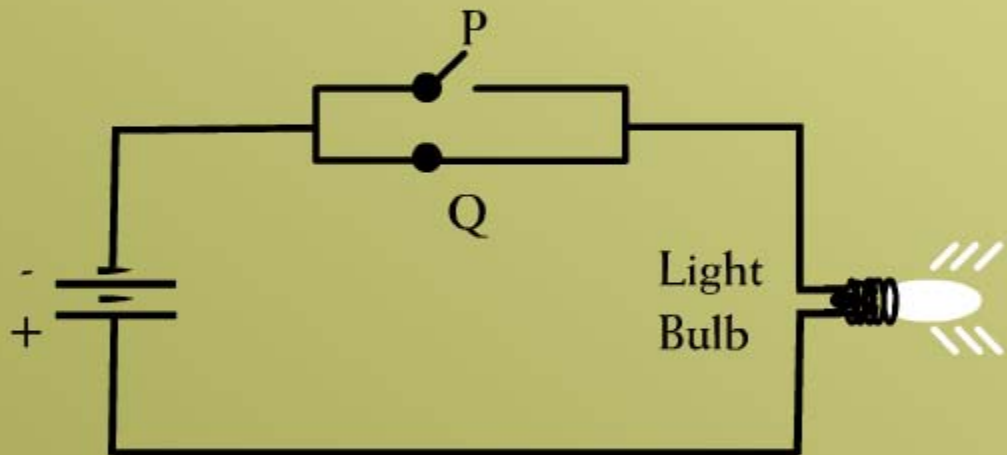

SWITCHES IN SERIES

Switches		Light Bulb
P	Q	State
T	T	T
T	F	F
F	T	F
F	F	F

P	Q	$P \wedge Q$
T	T	T
T	F	F
F	T	F
F	F	F


SWITCHES IN PARALLEL

Switches		Light Bulb
P	Q	State
T	T	T
T	F	T
F	T	T
F	F	F

P	Q	$P \vee Q$
T	T	T
T	F	T
F	T	T
F	F	F

NOT GATE OR INVERTER

Input	Output
P	Q
1	0
0	1

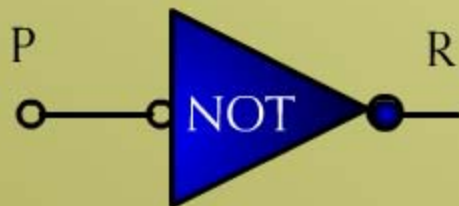

AND GATE

Input		Output
P	Q	R
1	1	1
1	0	0
0	1	0
0	0	0




OR GATE


Input		Output
P	Q	R
1	1	1
1	0	1
0	1	1
0	0	0



COMBINATIONAL CIRCUIT

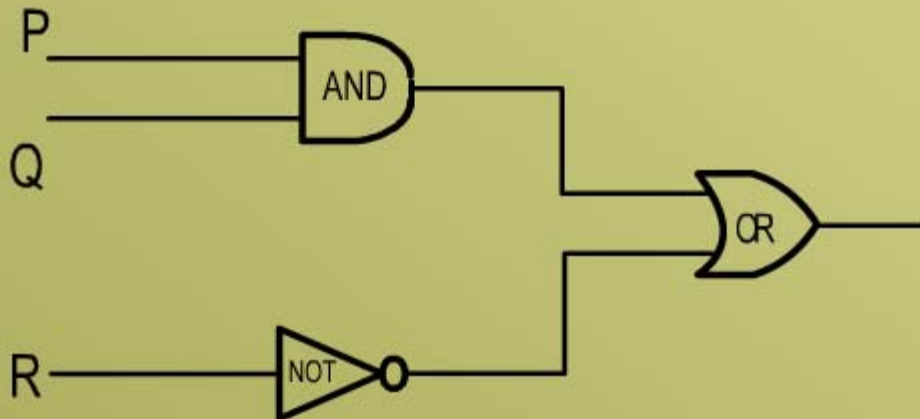

OUTPUT FOR A GIVEN INPUT

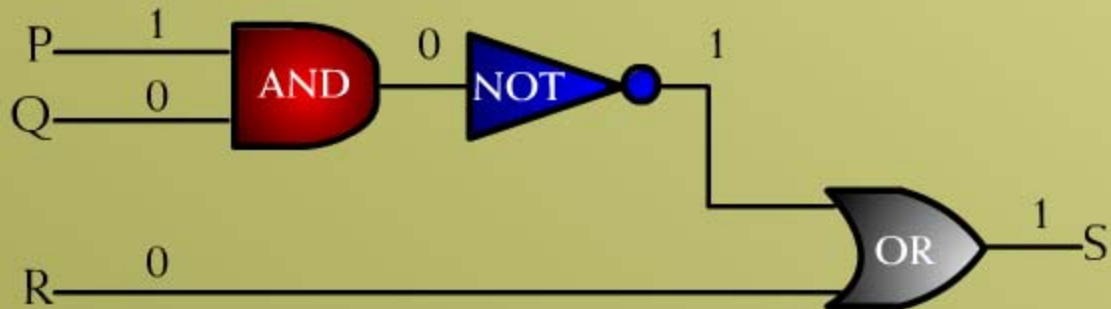

INPUT/OUTPUT TABLE FOR A CIRCUIT

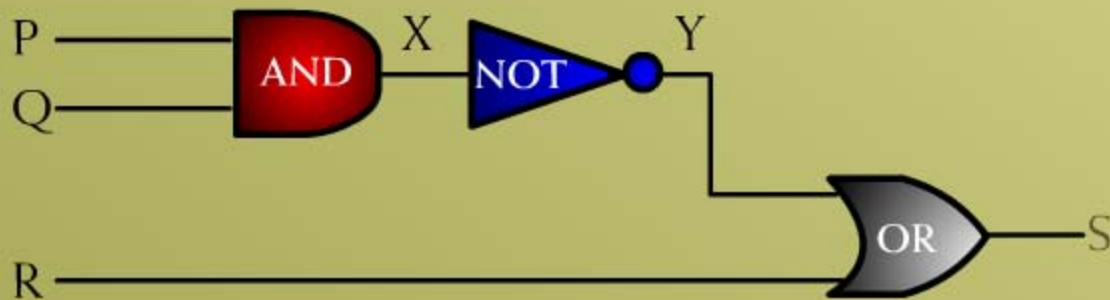


TABLE FOR CIRCUIT

P	Q	R	X	Y	S
1	1	1			
1	1	0			
1	0	1			
1	0	0			
0	1	1			
0	1	0			
0	0	1			
0	0	0			

TABLE FOR CIRCUIT

P	Q	R	X	Y	S
1	1		1		
1	1		1		
1	0		0		
1	0		0		
0	1		0		
0	1		0		
0	0		0		
0	0		0		


TABLE FOR CIRCUIT

[illegible]


TABLE FOR CIRCUIT

P	Q	R	X	Y	S
		1		0	1
		0		0	0
		1		1	1
		0		1	1
		1		1	1
		0		1	1
		1		1	1
		0		1	1

BOOLEAN EXPRESSION FOR A CIRCUIT

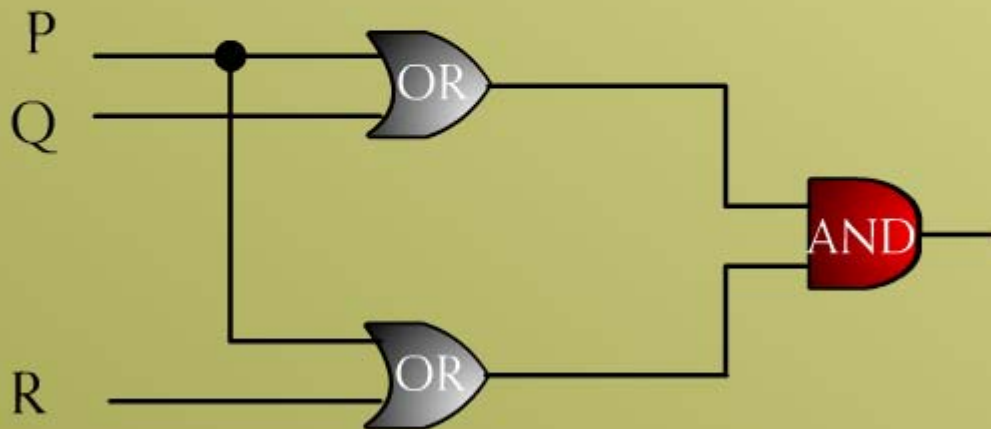


BOOLEAN EXPRESSION FOR A CIRCUIT

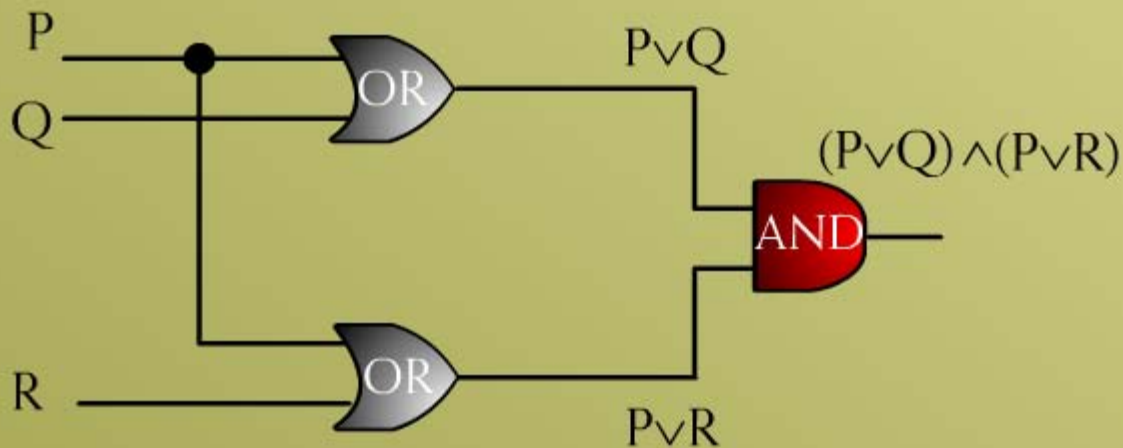

CIRCUIT FOR A BOOLEAN EXPRESSION

$$(P \wedge Q) \vee \sim R$$

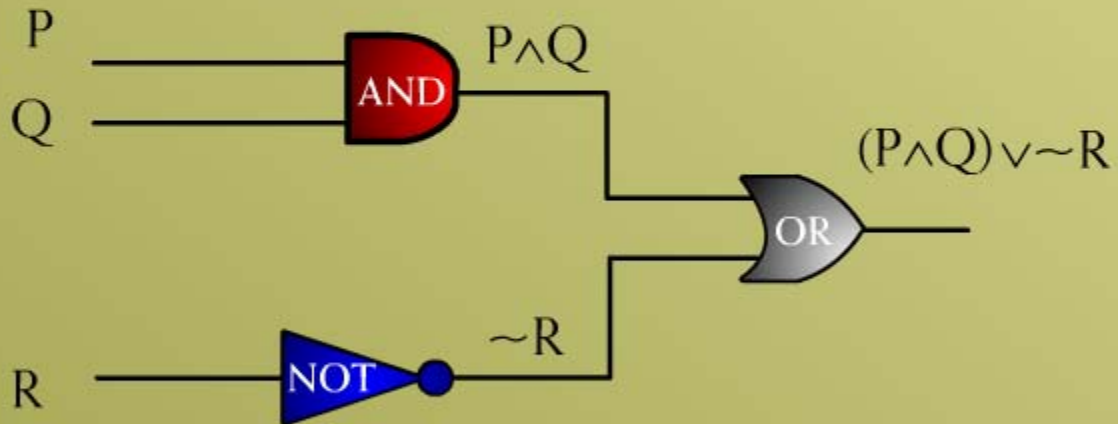

CIRCUIT FOR INPUT/OUTPUT TABLE

INPUTS			OUTPUTS
P	Q	R	S
1	1	1	0
1	1	0	1
1	0	1	0
1	0	0	0
0	1	1	1
0	1	0	0
0	0	1	0
0	0	0	0

SOLUTION

INPUTS			OUTPUTS
P	Q	R	S
1	1	1	0
1	1	0	1
1	0	1	0
1	0	0	0
0	1	1	1
0	1	0	0
0	0	1	0
0	0	0	0

$$P \wedge Q \wedge \sim R$$




$$\sim P \wedge Q \wedge R$$



CIRCUIT DIAGRAM
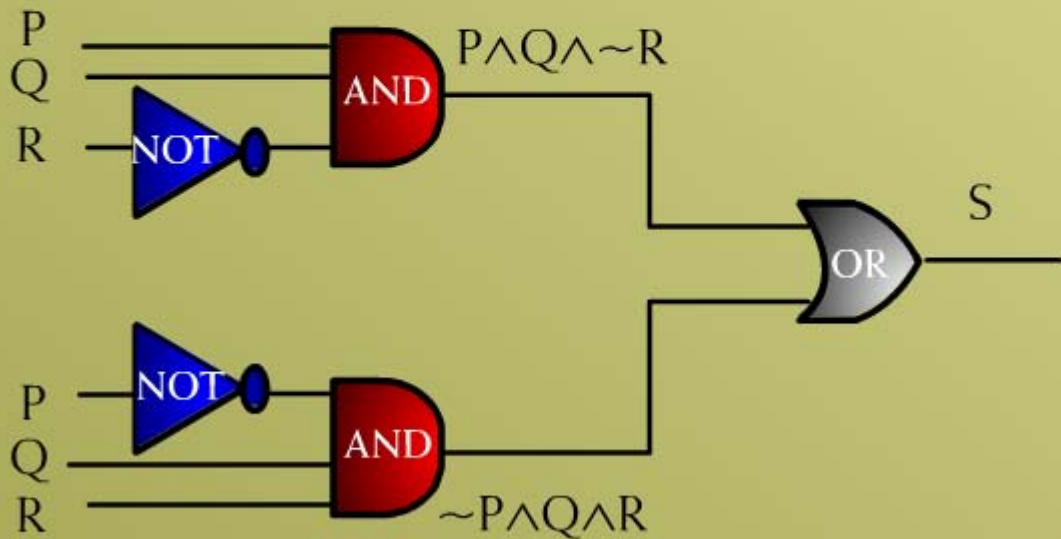
$$(P \wedge Q \wedge \sim R) \vee (\sim P \wedge Q \wedge R) = S$$



EXERCISE

Design a circuit to take **input** signals **P**, **Q**, and **R** and **output** a **1** if, and only if, **P** and **Q** have the same value and **Q** and **R** have opposite values.

EXERCISE

INPUTS			OUTPUTS
P	Q	R	S
1	1	1	0
1	1	0	1
1	0	1	0
1	0	0	0
0	1	1	0
0	1	0	0
0	0	1	1
0	0	0	0

$$P \wedge Q \wedge \sim R$$




$$\sim P \wedge Q \wedge R$$




Solution contd..

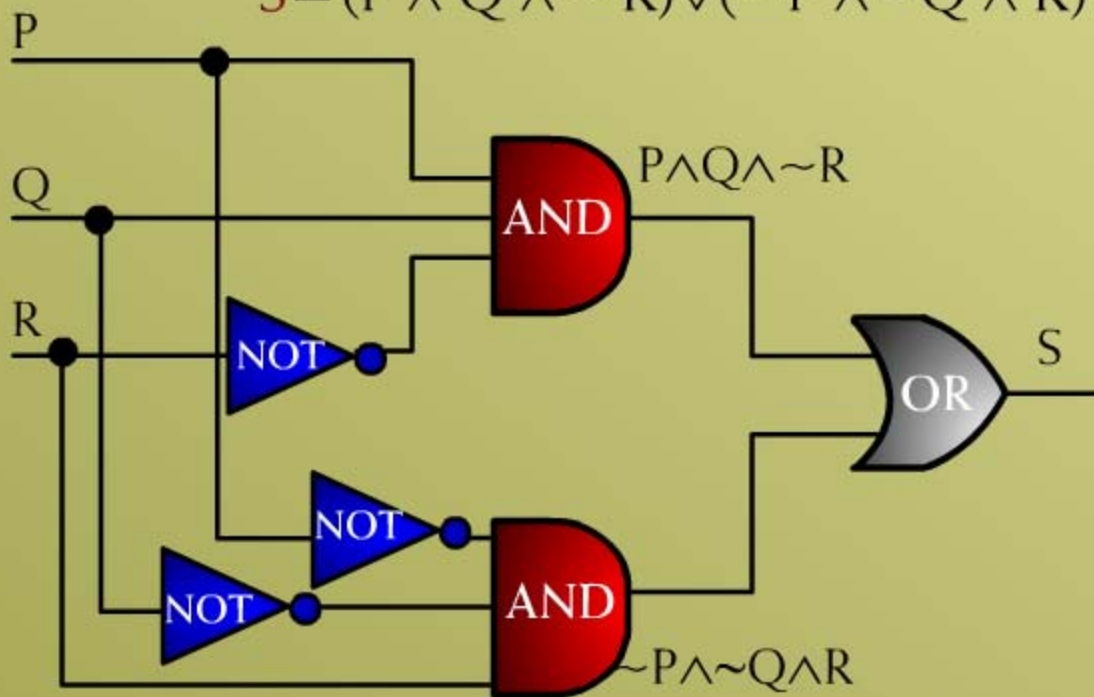
$$S = (P \wedge Q \wedge \sim R) \vee (\sim P \wedge \sim Q \wedge R)$$



EXERCISE

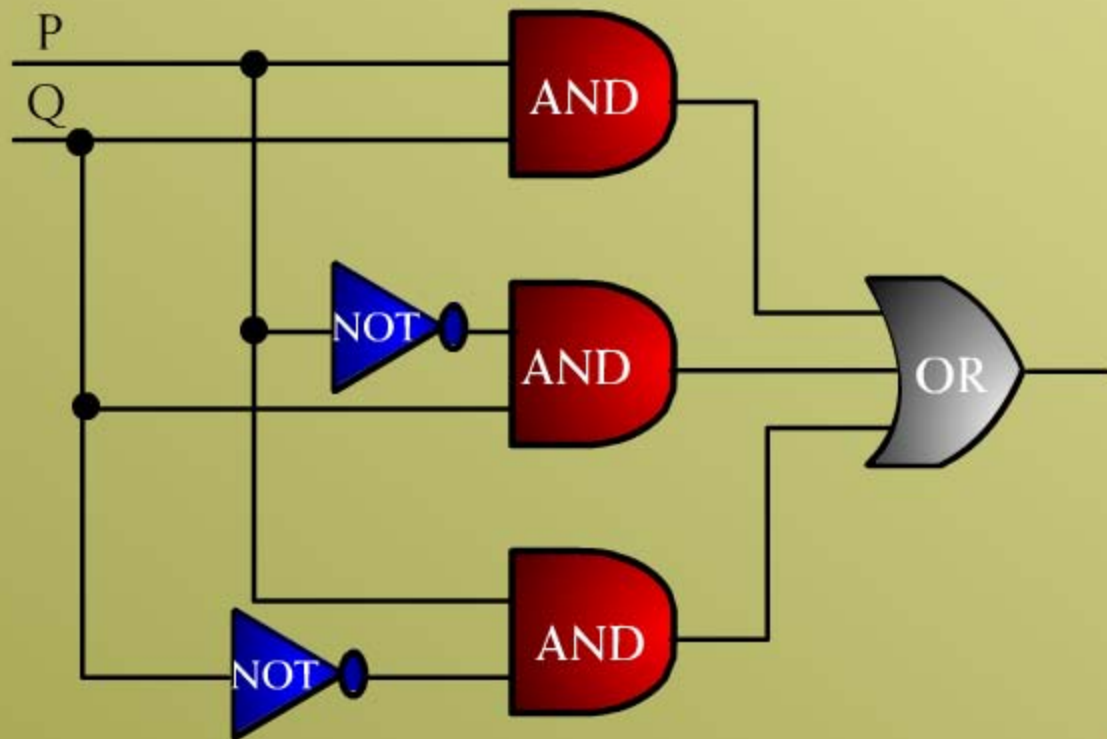

SOLUTION

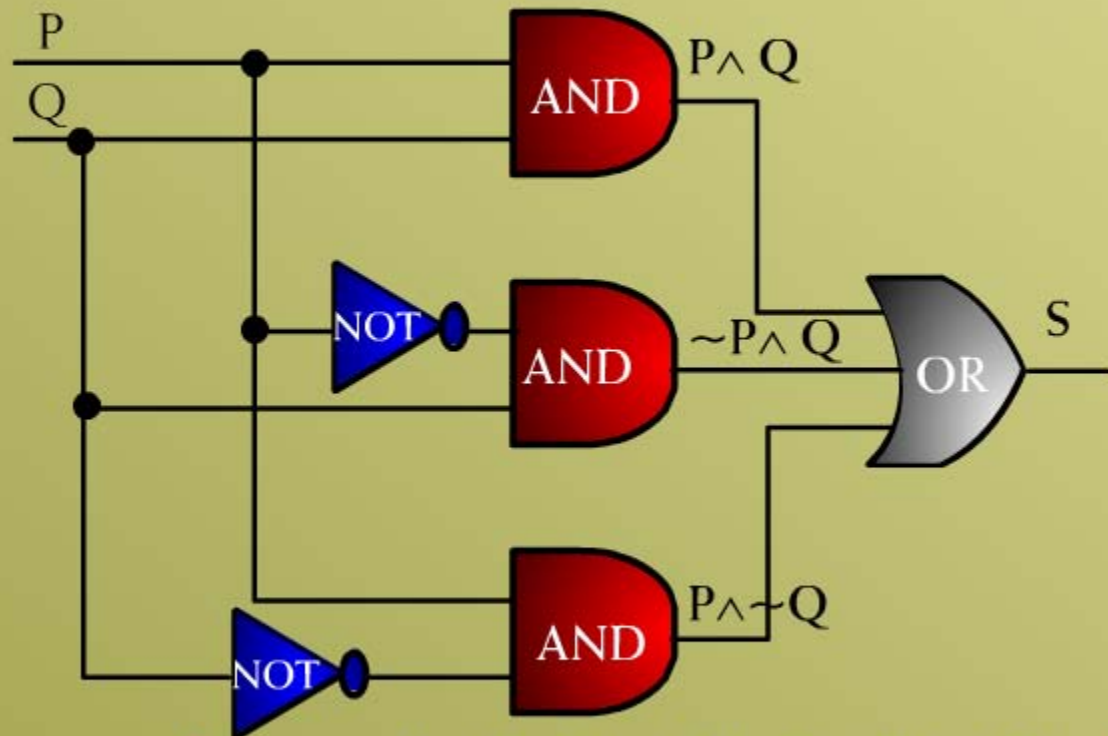

Output: $S = (P \wedge Q) \vee (\sim P \wedge Q) \vee (P \wedge \sim Q)$

Solution contd..

Statement	Reason
$(P \wedge Q) \vee (\sim P \wedge Q) \vee (P \wedge \sim Q)$	
$\equiv (P \wedge Q) \vee (\sim P \wedge Q) \vee (P \wedge \sim Q)$	
$\equiv (P \vee \sim P) \wedge Q \vee (P \wedge \sim Q)$	Distributive law
$\equiv t \wedge Q \vee (P \wedge \sim Q)$	Negation law
$\equiv Q \vee (P \wedge \sim Q)$	Identity law
$\equiv (Q \vee P) \wedge (Q \vee \sim Q)$	Distributive law

Solution contd..

Statement	Reason
$\equiv (Q \vee P) \wedge t$	Negation law
$\equiv Q \vee P$	Identity law
$\equiv Q \vee P$	Commutative law

Thus $(P \wedge Q) \vee (\sim P \wedge Q) \vee (P \wedge \sim Q) \equiv P \vee Q$